



### TIP31 AG|C Transistor used as a switch

- The Arduino, Tip31, and LED(s) must share a common ground.

“By putting a small voltage and current on the Base (1) you allow a larger current to flow from the Collector (2) to the Emitter (3).”

- p.99 of Physical Computing by Tom Igoe